 


1. Write the VHDL Code for a 3-to-8 Binary Decoder, with Active Low outputs and with an Active Low strobe enable.

**THIS TIME USE BEHAVIORAL MODELS (with a "Process") FOR YOUR VHDL DESCRIPTIONS. Compose 4 different Behavioral Models:**

- Using one IF-THEN-ELSIF-ELSE statement (inside a process) to describe the entire 3-to-8 Decoder device.
- Using an IF-THEN-ELSIF-ELSE statement for the decoder logic (how the "B" inputs affect the outputs), inside of an IF-THEN-ELSE statement for the Enable logic (how "EN\_L" affects the outputs). ["Nested" IF statements]
- Using both a CASE statement and an "IF" statement in a single description for this device. Use the CASE statement for the decoder logic (how the "B" inputs affect the outputs), inside of an IF-THEN-ELSE statement for the Enable logic (how "EN\_L" affects the outputs). [CASE nested inside an IF]
- Using separate CASE and IF statements in a single process for this device. This time the CASE should not be inside the IF statement; nor should the IF be inside the CASE statement (*i.e.* no nesting of statements.)



*So the point here was to show you that there are many different ways to describe the same device in VHDL; and to help you learn all the different programming constructs available to you.*

EN'	B2	B1	B0	F0'	F1'	F2'	F3'	F4'	F5'	F6'	F7'
0	0	0	0	0	1	1	1	1	1	1	1
0	0	0	1	1	0	1	1	1	1	1	1
0	0	1	0	1	1	0	1	1	1	1	1
0	0	1	1	1	1	1	0	1	1	1	1
0	1	0	0	1	1	1	1	0	1	1	1
0	1	0	1	1	1	1	1	1	0	1	1
0	1	1	0	1	1	1	1	1	1	0	1
0	1	1	1	1	1	1	1	1	1	1	0
1	-	-	-	1	1	1	1	1	1	1	1

entity BinaryDecoder3to8 is

```
Port ( Binary_In : in  STD_LOGIC_VECTOR (2 downto 0);
      Enable_L: in STD_LOGIC; -- active low
      Decode_Out_L : out STD_LOGIC_VECTOR (7 downto 0)); --active low
end BinaryDecoder3to8;
```

a) Using one IF-THEN-ELSIF-ELSE statement (inside a process) to describe the device.

architecture Behavioral of BinaryDecoder3to8 is

```
signal Enable: STD_LOGIC; -- active high version
signal Decode_Out : STD_LOGIC_VECTOR (7 downto 0); -- active high version
begin
```

-- Using a Behavioral Description (Process)

decoder\_behav: process (Binary\_In, Enable) is

begin

-- Handle the Enable first

```
if (Enable = '0') then Decode_Out <= "00000000";
```

-- If enabled, then decode the input

```
elseif (Binary_In = "111") then Decode_Out <= "10000000";
elseif (Binary_In = "110") then Decode_Out <= "01000000";
elseif (Binary_In = "101") then Decode_Out <= "00100000";
elseif (Binary_In = "100") then Decode_Out <= "00010000";
elseif (Binary_In = "011") then Decode_Out <= "00001000";
elseif (Binary_In = "010") then Decode_Out <= "00000100";
elseif (Binary_In = "001") then Decode_Out <= "00000010";
elseif (Binary_In = "000") then Decode_Out <= "00000001";
else
    Decode_Out <= "00000000";
end if;
```

end process decoder\_behav;

-- Convert to active low Enable and outputs

```
Enable <= not( Enable_L); -- This MUST be OUTSIDE the process.
```

```
Decode_Out_L <= not(Decode_Out); -- This MUST be OUTSIDE the process.
```

end Behavioral;

----- OR -----  
(Alternative solution)

architecture Behavioral of BinaryDecoder3to8 is

signal Enable: STD\_LOGIC;

signal Decode\_Out : STD\_LOGIC\_VECTOR (7 downto 0);

begin

-- Using a Behavioral Description (Process)

decoder\_behav: process (Binary\_In, Enable) is

begin

-- Set up a "default" that handles most output bits

Decode\_Out <= "00000000"; -- we can get away with this in a process!

-- Handle the not Enabled case first

if (Enable = '0') then Decode\_Out <= "00000000";

-- else, Only change the 1 specific bit that is selected

-- (relying on the values provided above for the other bits)

elsif (Binary\_In = "111") then Decode\_Out(7) <= '1';

elsif (Binary\_In = "110") then Decode\_Out(6) <= '1';

elsif (Binary\_In = "101") then Decode\_Out(5) <= '1';

elsif (Binary\_In = "100") then Decode\_Out(4) <= '1';

elsif (Binary\_In = "011") then Decode\_Out(3) <= '1';

elsif (Binary\_In = "010") then Decode\_Out(2) <= '1';

elsif (Binary\_In = "001") then Decode\_Out(1) <= '1';

elsif (Binary\_In = "000") then Decode\_Out(0) <= '1';

else Decode\_Out <= "00000000";

end if;

end process decoder\_behav;

-- Convert to active low Enable and outputs

Enable <= not( Enable\_L); -- This MUST be OUTSIDE the process.

Decode\_Out\_L <= not(Decode\_Out); -- This MUST be OUTSIDE the process.

end Behavioral;

b) Using an IF-THEN-ELSIF-ELSE statement for the decoder logic (how the “B” inputs affect the outputs), inside of an IF-THEN-ELSE statement for the Enable logic (how “EN” affects the outputs).

architecture NestedBehavioral of BinaryDecoder3to8 is

signal Enable: STD\_LOGIC;

signal Decode\_Out : STD\_LOGIC\_VECTOR (7 downto 0);

begin

decoder\_behav: process (Binary\_In, Enable) is

begin

-- Handle the Enable first

if (Enable = '0') then Decode\_Out <= "0000000"; -- if disabled  
else

-- If enabled, decode the input

```
if      (Binary_In = "111") then Decode_Out <= "10000000";
elsif   (Binary_In = "110") then Decode_Out <= "01000000";
elsif   (Binary_In = "101") then Decode_Out <= "00100000";
elsif   (Binary_In = "100") then Decode_Out <= "00010000";
elsif   (Binary_In = "011") then Decode_Out <= "00001000";
elsif   (Binary_In = "010") then Decode_Out <= "00000100";
elsif   (Binary_In = "001") then Decode_Out <= "00000010";
elsif   (Binary_In = "000") then Decode_Out <= "00000001";
else    Decode_Out <= "00000000";
```

end if;

end if;

end process decoder\_behav;

-- Convert to active low Enable and outputs

Enable <= not( Enable\_L); -- This MUST be OUTSIDE the process;

Decode\_Out\_L <= not(Decode\_Out); -- This MUST be OUTSIDE the process;

end NestedBehavioral;

----- OR -----  
(Alternative solution)

architecture NestedBehavioral2 of BinaryDecoder3to8 is

signal Enable: STD\_LOGIC;

signal Decode\_Out : STD\_LOGIC\_VECTOR (7 downto 0);

begin

decoder\_behav: process (Binary\_In, Enable) is

begin

-- Handle the Enable first

if (Enable = '1')

then -- If enabled, decode the input

```
if      (Binary_In = "111") then Decode_Out <= "10000000";
elsif   (Binary_In = "110") then Decode_Out <= "01000000";
elsif   (Binary_In = "101") then Decode_Out <= "00100000";
elsif   (Binary_In = "100") then Decode_Out <= "00010000";
elsif   (Binary_In = "011") then Decode_Out <= "00001000";
elsif   (Binary_In = "010") then Decode_Out <= "00000100";
elsif   (Binary_In = "001") then Decode_Out <= "00000010";
elsif   (Binary_In = "000") then Decode_Out <= "00000001";
else
        Decode_Out <= "00000000";
end if;
```

else Decode\_Out <= "00000000"; -- if not enabled

end if;

end process decoder\_behav;

-- Convert to active low Enable and outputs

Enable <= not( Enable\_L); -- This MUST be OUTSIDE the process;

Decode\_Out\_L <= not(Decode\_Out); -- This MUST be OUTSIDE the process;

end NestedBehavioral2;

- c) Using both a CASE statement and an “IF” statement in a single description for this device. Use the CASE statement for the decoder logic (how the “B” inputs affect the outputs), inside of an IF-THEN-ELSE statement for the Enable logic (how EN’ affects the outputs). [ CASE nested inside an IF]

architecture Behavioral of BinaryDecoder3to8 is

signal Enable: STD\_LOGIC;

signal Decode\_Out : STD\_LOGIC\_VECTOR (7 downto 0);

begin

-- Using a Behavioral Description (Process)

decoder\_behav: process (Binary\_In, Enable) is

begin

-- Handle the Enable first

if (Enable = '0') then Decode\_Out <= "00000000";

else

-- If enabled, decode the input

case (Binary\_In) is

when "111" => Decode\_Out <= "10000000";

when "110" => Decode\_Out <= "01000000";

when "101" => Decode\_Out <= "00100000";

when "100" => Decode\_Out <= "00010000";

when "011" => Decode\_Out <= "00001000";

when "010" => Decode\_Out <= "00000100";

when "001" => Decode\_Out <= "00000010";

when "000" => Decode\_Out <= "00000001";

when others => Decode\_Out <= "00000000";

end case;

end if;

end process decoder\_behav;

-- Convert to active low Enable and outputs

Enable <= not( Enable\_L);

Decode\_Out\_L <= not( Decode\_Out );

end Behavioral;

*[NOTE: The Xilinx VHDL compiler produced an identical circuit implementation for this Behavioral VHDL code as was generated in Assignment #12 from a Concurrent (Data-Flow) VHDL model. (This is a "good" thing!) The code above is actually a pretty well-constructed, understandable description of a decoder.]*

- d) Using separate CASE and IF statements in a single process for this device. This time the CASE should not be inside the IF statement; nor should the IF be inside the CASE statement (*i.e.* no nesting of statements.)

architecture Behavioral of BinaryDecoder3to8 is

```
signal Enable: STD_LOGIC;
signal Decode_Out : STD_LOGIC_VECTOR (7 downto 0);
```

```
begin
```

```
-- Using a Behavioral Description (Process)
```

```
decoder_behav: process (Binary_In, Enable) is
```

```
begin
```

```
-- decoder the input
```

```
case (Binary_In) is
```

```
when "111" => Decode_Out <= "10000000";
```

```
when "110" => Decode_Out <= "01000000";
```

```
when "101" => Decode_Out <= "00100000";
```

```
when "100" => Decode_Out <= "00010000";
```

```
when "011" => Decode_Out <= "00001000";
```

```
when "010" => Decode_Out <= "00000100";
```

```
when "001" => Decode_Out <= "00000010";
```

```
when "000" => Decode_Out <= "00000001";
```

```
when others => Decode_Out <= "00000000";
```

```
end case;
```

```
-- Handle the Enable LAST! in the process
```

```
if (Enable = '0')
```

```
then Decode_Out <= "00000000";
```

```
end if;
```

```
end process decoder_behav;
```

```
-- Convert to active low Enable and outputs
```

```
Enable <= not( Enable_L);
```

```
Decode_Out_L <= not(Decode_Out);
```

```
end Behavioral;
```

*This version is a little trickier than the previous VHDL solutions. Here we are relying on the peculiar behavior of statements inside a PROCESS. For multiple assignments to the same signal inside of a process, only the last assignment made will take effect. Therefore, if the decoder is enabled (Enable = 1), then the final*

```
then Decode_Out <= "00000000";
```

*will never take place. However, if the decoder is not enabled (Enable=0), then this code will run and “cancel out” the decoding logic results from the CASE statement above this point in the PROCESS.*

*This is also one case where we can get away with not using an “ELSE”, since the CASE statement tells VHDL what to do with Decode\_Out for all other possibilities (when Enable ≠ 0).*